

The circuit diagram illustrates a precision instrumentation amplifier configuration using three $\frac{1}{2}$ OPA1013 op-amp sections. The power supply is V_+ (4.5V to 36V). A current source, labeled $\frac{1}{2}$ REF200, provides a $100\mu\text{A}$ current to the non-inverting input of the first op-amp (A_1). The input voltage is 0.5V , and a $5\text{ k}\Omega$ resistor (R_3) is connected to ground. The feedback resistor for A_1 is $R_1 = 1\text{ k}\Omega$. The output of A_1 is $V_{REF1} = 3.4\text{V}$. The second op-amp (A_2) is configured as a voltage follower with its output $V_{REF2} = 0.5\text{V}$. The feedback resistor for A_2 is $R_2 = 5.8\text{ k}\Omega$. The third op-amp (A_3) is configured as a differential amplifier with its non-inverting input connected to the V_{IN} signal. The feedback resistor for A_3 is $R_4 = 10\text{ k}\Omega$. The output of A_3 is V_{OUT} . The fourth op-amp (A_4) is configured as a voltage follower with its output V_{OUT} . The feedback resistor for A_4 is $R_5 = 10\text{ k}\Omega$. The output of A_4 is V_{OUT} . The feedback resistor for A_4 is $R_6 = 10\text{ k}\Omega$. The output of A_4 is V_{OUT} . The feedback resistor for A_4 is $R_7 = 10\text{ k}\Omega$. The output of A_4 is V_{OUT} .

Chapter 5 - Analog-to-Digital and Digital-to-Analog Conversions

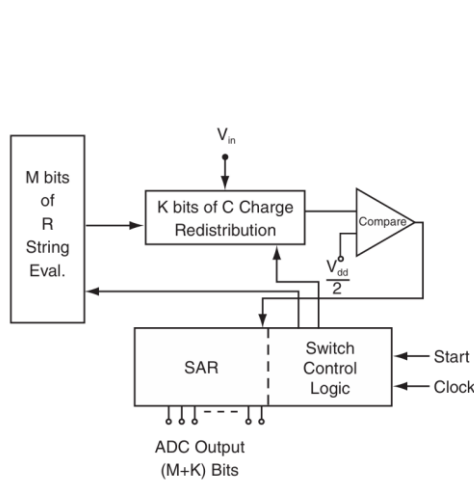


Figure 5-10: Hybrid R-tree capacitor charge-redistribution ADC

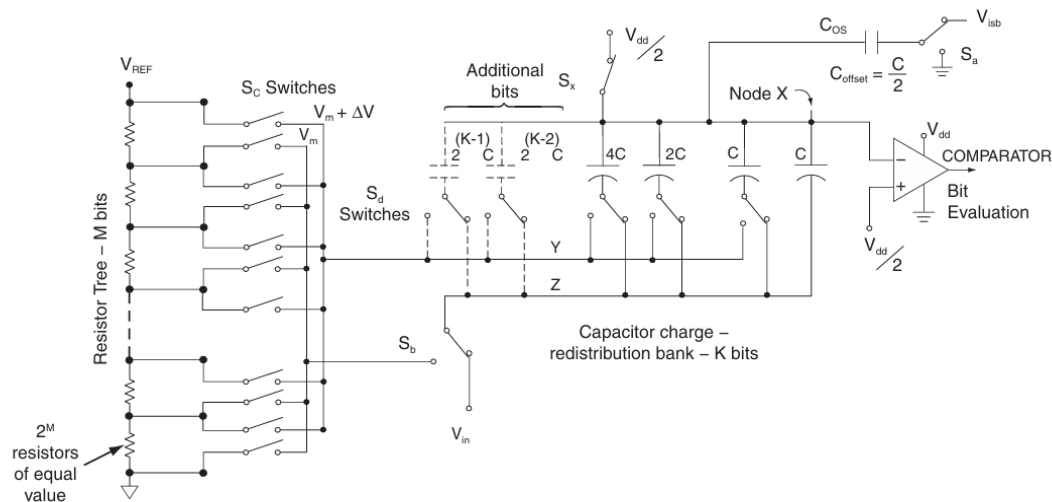


Figure 5-11: Details of resistor tree and capacitor bank (data acquisition period)

Pada sebuah sistem 'Hybrid R-tree Capacitor Charge-Redistribution ADC'. Proses konversi beresolusi tinggi ini sangat bergantung pada prinsip konservasi muatan. Manakah sumber kesalahan non-linearitas (non-linearity) yang paling fundamental dan sulit dikompensasi yang timbul dari pengoperasian saklar-saklar (switches) capacitor bank itu sendiri selama proses evaluasi bit?

- A. Ketidakcocokan (mismatch) kapasitansi parasitik gate-to-source dan gate-to-drain pada saklar-saklar
- B. Kebocoran muatan (charge leakage) melalui saklar yang 'off' (posisi terbuka)
- C. Derau (noise) kT/C yang dihasilkan oleh saklar-saklar saat ditutup
- D. Resistansi 'On' (R_{on}) yang konstan namun tidak nol dari saklar-saklar
- E. Injeksi muatan (charge injection) dan clock feedthrough dari saklar-saklar, di mana jumlah muatannya bergantung pada level tegangan sinyal input

Penjelasan:

Jawaban “E”

Ketika saklar (transistor) mati, ia menginjeksikan sejumlah muatan dari salurannya, dan jumlah ini dapat bervariasi tergantung pada tegangan sinyal, sehingga menciptakan kesalahan non-linier yang bergantung pada sinyal.